

Amplifier

- used to amplify signals so that they can be measured.



$$\frac{V_{out}}{\Delta V_{in}} = A_v \quad A_v \rightarrow \text{voltage gain}$$

(big)

A_v - linear (at all frequencies)

$$\frac{V_{in}}{I_{in}} = \frac{Z_{in}}{I_{in}} \quad \text{(Big)}$$

$$\frac{V_{out}}{I_{out}} = \frac{Z_{out}}{I_{out}} \quad \text{(small)}$$

↓


V_{out} ≈ small

does not affect the current in the load


Operational amplifier (Op-amp)

- integrated circuit (resistors, capacitors, BJTs ...)
- manufactured as a single chip of silicon
- building block
 - amplifier
 - integrator
 - summer
 - differentiator
 - comparator
 - Analog to Digital / Digital to Analog converters
 - sample & hold amplifiers
(e.g. LCD display)

LM 741

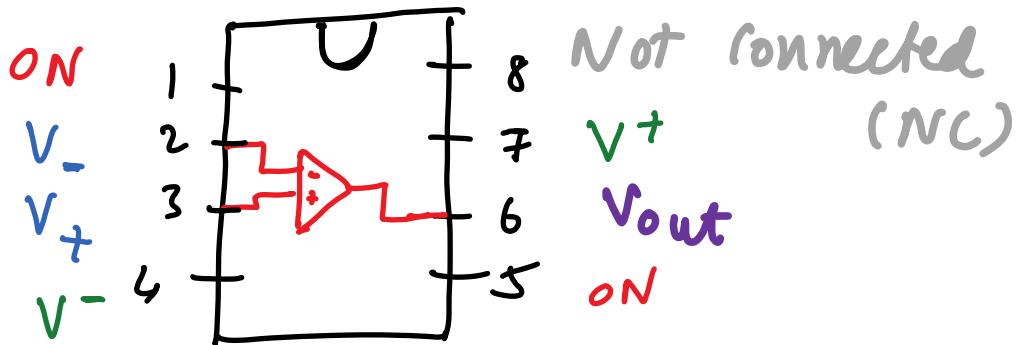

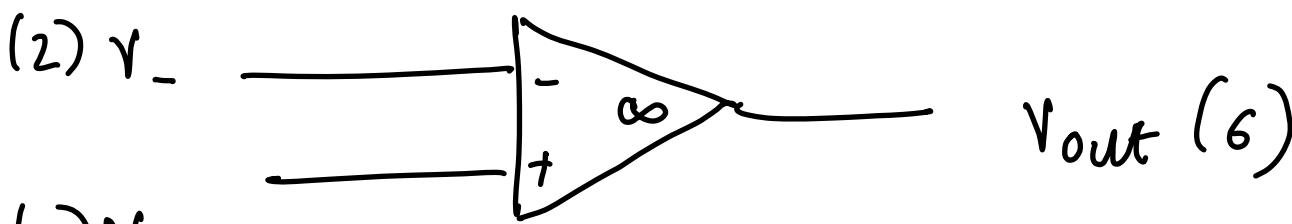
- ON - offset Null
 - V_-, V_+ - inputs
 - V^-, V^+ - supply voltages (external voltage)
 $+15V, -15V$
 - V_{out} - output voltage
- 2, 3, 6 - circuit diagrams




(2) V_-
(3) V_+

open-loop (op-amp) [unstable]
X used sometimes.


Negative feedback (Stable)

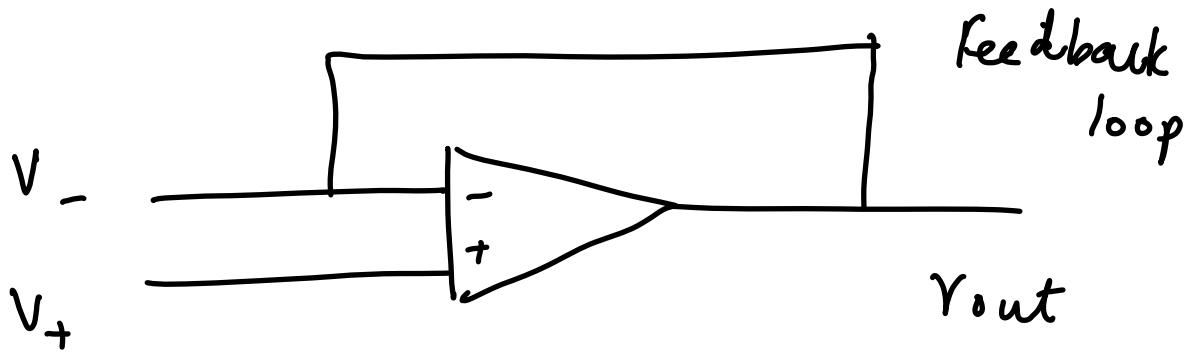

Positive feedback (Unstable)

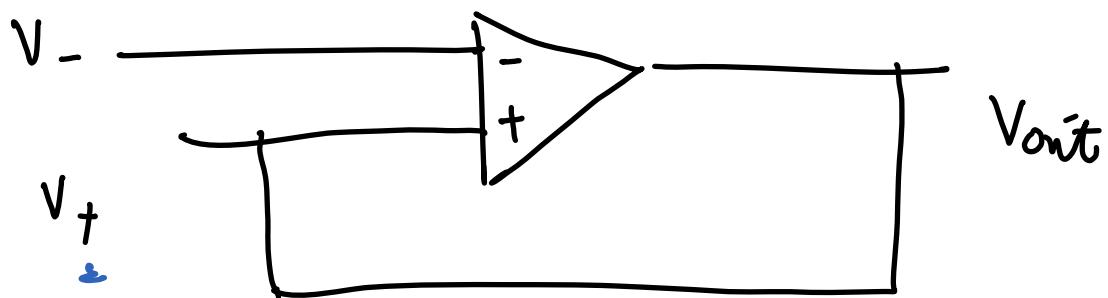

Ideal op-amp model

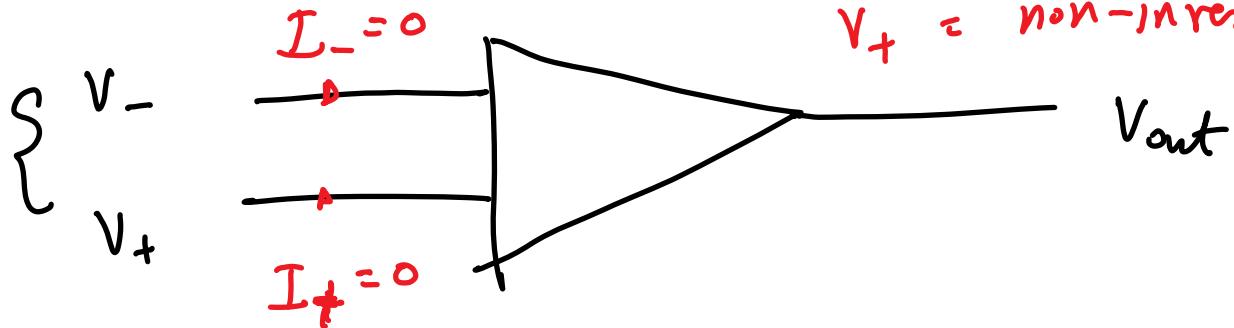

V_- = inverting input
 V_+ = non-inverting input

- ① $I_- = 0 \quad \& \quad I_+ = 0$
- ② $V_+ = V_-$

(As $Z_{in} \rightarrow \infty$)

(As $A_V \rightarrow \infty$)

$$\frac{V_{out}}{\Delta V_{in}} = A_V$$

- ③ $t_{out} = 0$


$$\frac{V_{out}}{V_+ - V_-} = A_V \rightarrow \infty$$

V_{out} does
not depend on
 I_{out}


$$V_{out} = A_V (V_+ - V_-)$$

\uparrow finite	\uparrow ∞	\uparrow 0
----------------------	------------------------	-----------------

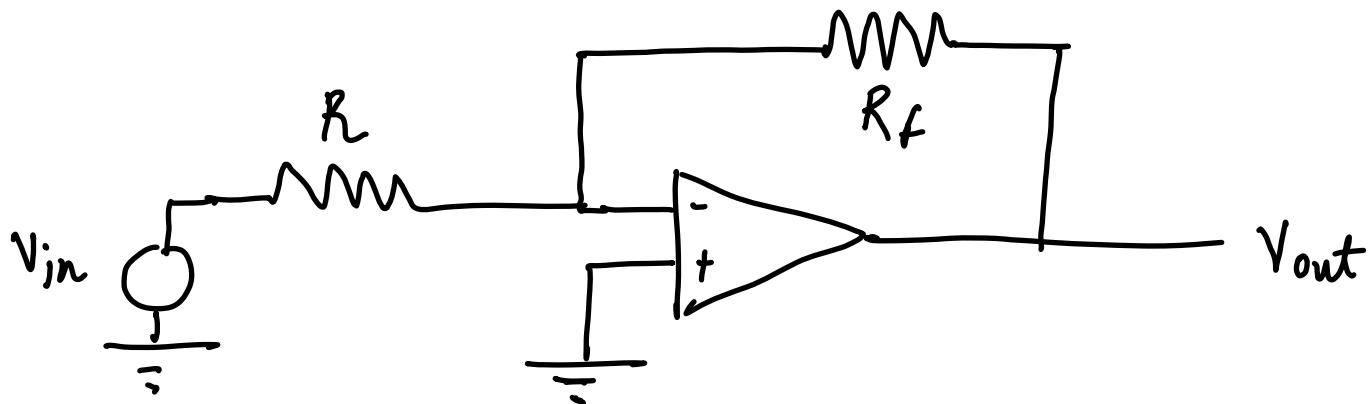① Inverting amplifier
(-ive) (increase amplitude)



$$\frac{V_{out}}{V_{in}} = ?$$

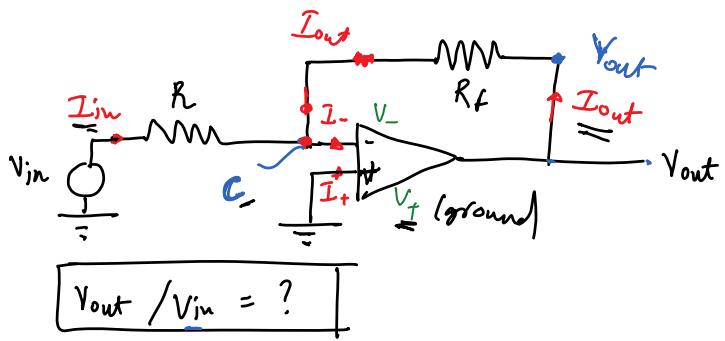

Assumptions for op-amp: $V_+ = V_-$
 $\Rightarrow I_- = I_+ = 0$

$$\begin{aligned} V_{out} - V_c &= I_{out} R_f \\ V_{in} - V_c &= I_{in} R \end{aligned} \quad \left[\frac{V_{out}}{V_{in}} = \frac{I_{out} R_f}{I_{in} R} \right]$$

$$V_+ = 0 \Rightarrow V_- = V_+ \Rightarrow V_- = 0$$

$$V_c = V_- \Rightarrow V_c = 0$$

At C: $I_{in} + I_{out} = I_- = 0$

$I_{out} = -I_{in} \Rightarrow \frac{I_{out}}{I_{in}} = -1$

$$\frac{I_{out}}{I_{in}} = 1 \quad || \quad \frac{V_{out}}{V_{in}} = \frac{I_{out}}{I_{in}} \frac{R_f}{R}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -\frac{R_f}{R}}$$

① $V_{out} = -\frac{R_f}{R} V_{in}$

\uparrow
inverting

② $R_f = 10^3 R$

$$\frac{V_{out}}{V_{in}} = -10^3 \text{ (amplification)}$$